



Exhibit F

(7 of 12)

Timing closure

Conventional way: Worst case delay sets timing

 
 
- 99% of paths meets timing, 1% does not
- Cell sizes do not change during Place and Route
- Design conservatively to avoid excessive iterations. Also WLM is tuned conservatively.
- This **oversizes** all cells
 - ◆ because also cells on non-critical paths are sized up.
- Chip significantly bigger than necessary (10-30%)



size + parasitics = timing

What about In-place optimization?

Timing closure

 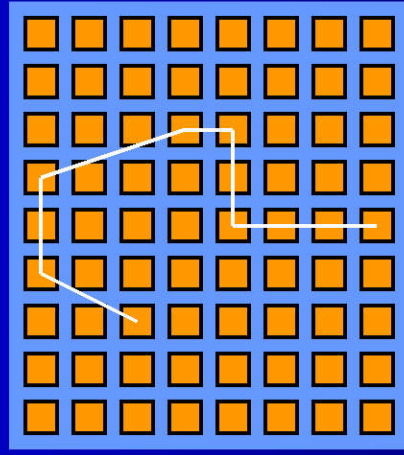


- Do a post-placement ECO,
- Change only the cells on the critical paths.
- Conservatism is still required because of limited ECO capacity.
- All non-critical cells are still oversized
- Chip still bigger than necessary.

size + parasitics = timing

Gain based synthesis: area is additive


Timing closure

timing + parasitics = size

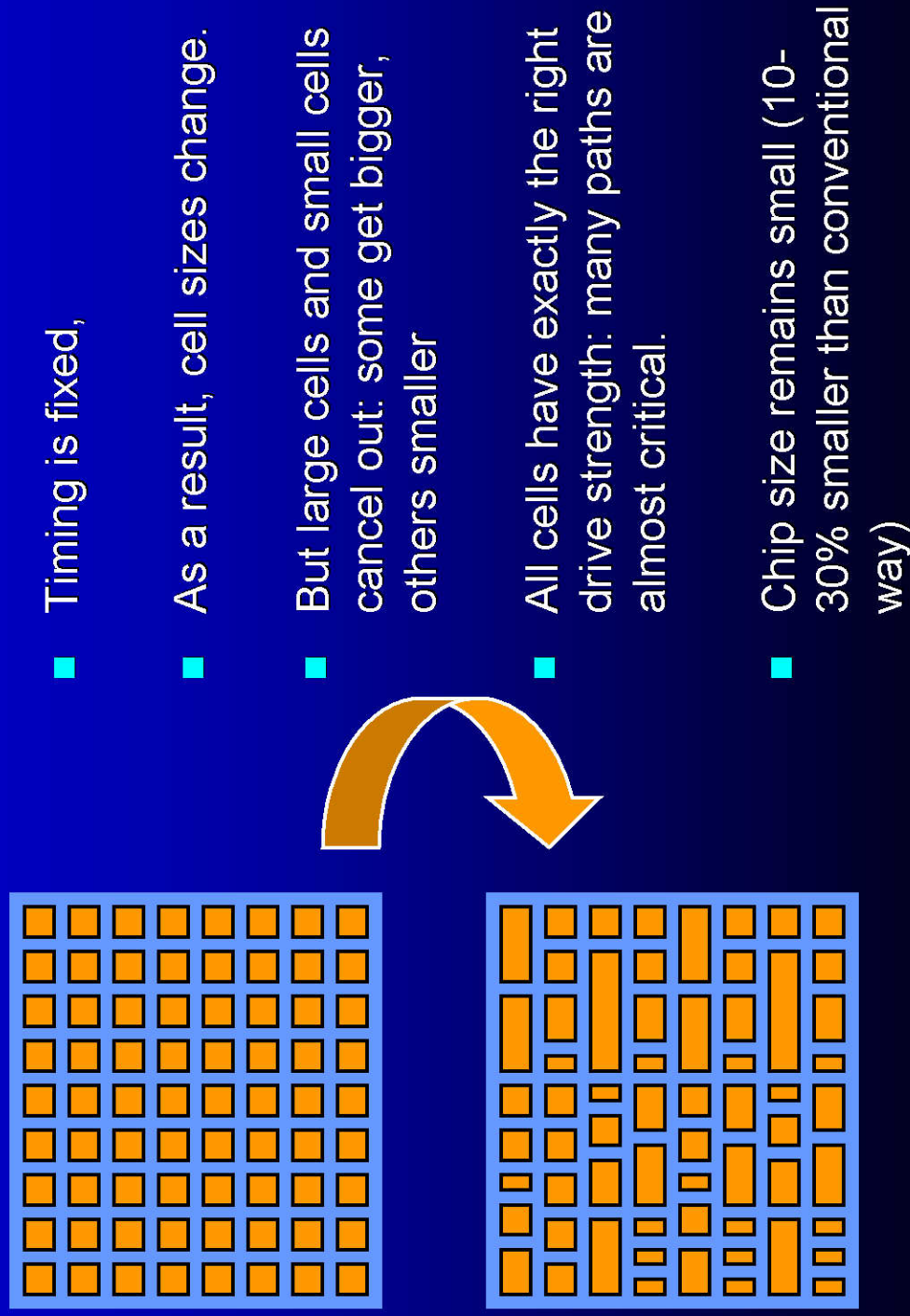

Logic (wireload) Synthesis

 - For a simple function $(A' + B) * C$
- Various logic structures are possible with one size



- Conventional logic synthesis tool attempts to optimize the delay by:
 - ◆ Logic restructuring
 - ◆ Picking the proper sizes
- This is driven by a vague idea of the wire load


Timing closure

Many sizing combinations


Heuristics tradeoffs --
significantly slower than
equation-based constant
delay

Gain-based synthesis: supercells

 - Need a single 'super' cell representing all sizes in a logic function.



- Contains:
 - ◆ g, h, p
 - ◆ size-range

 

Gain-based mapping

- In timing-critical parts, the mapper picks super cells that have low parasitic delay and highest maximum drive strength.
- In non-critical parts, 'weaker' super cells can be used.
 - ◆ Pick cells that have potentially the smallest size.
- Insert buffers on high-fanout nets

Putting it together

- Map onto generic 'super cells' with flexible area.
- Optimize gains for all super cells such that maximum speed is achieved. ***This fixes all delays in the circuit!***
- *Give up* if the (optimally conditioned) circuit does not meet the given timing criteria.
- Perform 'sizing driven placement': keep delay constant by adapting cell size to parasitic capacitance of the wires. Parasitic wire delay is based on coarse routing of the wires.
- Fix remaining timing problems through buffering, cloning, restructuring.
- Update floor plan if the timing is still not met.
- For each supercell, pick the one standard cell that matches the required drive strength.
- Legalize the placement (a.k.a detailed placement)
- Perform final routing under delay constraints.

Timing closure